

**GURUDAS COLLEGE**  
**DEPARTMENT OF COMPUTER SCIENCE**  
**SEM – I**  
**PAPER –CMS-A-CC1-TH**

**Time: 1 hour**

**Full marks:30**

**Answer Question 1 and any four from Question 2 to 9**

1. **ANSWER ANY FOUR .** 1.5 X 4 = 6
  - a. What is a maxterm?
  - b. A staircase light is controlled by two switches, one at the top of the stairs another at the bottom of the stairs. Design a truth table for this system.
  - c. Subtract  $(0111)_2$  from  $(0011)_2$  using 1's complement method.
  - d. Show that bubbled NOR gate is equal to AND logic function.
  - e. Write down the Huntington postulates.
  - f. What is the difference between a pulse and clock?
  - g. What are non-weighted reflective codes? Give examples.
  - h. What is floating point representation?
  
2. What is Gray code? Design a circuit which converts 3 bit binary to gray code. 6
  
3.  $Y = \sum m(0,2,3,7,8,9,12,15) + \sum d(1,5,6)$ , Simplify the function using K-Map and write down the SOP. 6
  
4. Construct a JK flip flop using T flip flop. Show the steps clearly. 6
  
5. What is Race around condition? How can we prevent this? 2+4
  
6. Design a circuit that will convert 2-4-2-1 to Excess -3 code. 6
  
7. Design a 2 bit magnitude comparator. 6
  
8. Design 8x1 Multiplexer using 2x1 multiplexer. 6
  
9. Implement the function  $Y = \sum(0,2,3,5,8,10,12,14,15)$  using a 4x1 multiplexer and other logic gates. 6