GURUDAS COLLEGE INTERNAL EXAMINATION,2020 COMPUTER SCIENCE (HONOURS) (1+1+1 new regulations) Part I Paper I THEORY

F.M=100

Answer Question No. 1 and any 4 from the rest

Answer any four Questions (4x5) 1.

- a. Draw the Schmitt Trigger circuit with input and output diagram.
- b. What are the differences between ideal OPAMP and Practical OPAMP?
- c. What is meant by Duality in Boolean Algebra?
- d. What is the difference between a virus and Worm.
- e. Convert $(FACE)_{16} = ()_2 = ()_8$. State and explain De Morgan's Theorem.
- f. Distinguish between combinational and sequential circuit.
- Define instruction cycle? What is DMA? g.
- h. What is indirect addressing? How is it implemented.
- 2. a. Draw the Bridge Rectifier and explain the function
 - b. Discuss the effects of negative feedback. How does negative feedback introduce stability of gain?
 - c. Draw the output characteristic of an N-P-N transistor connected in common emitter mode and explain the different regions of its operations. [8+7+5]
- 3. a. What is memory partition ? how does it facilate in multiprogramming? Discuss briefly.
 - b. What is virtual memory? State advantages and limitations of virtual memory.
 - c. What do you mean by logical and physical address space?
 - d. Why is the shell is not part of a kernel?

[2+6+2+5+3+2]

- 4. a. Define multimedia. List out the building blocks of multimedia.
 - b. Briefly describe the main features that distinguish between micro computer, mini computer and main frame computer.
 - c. Write a short note on computer virus.
 - d. State differences between High level languages and low level languages.
 - e. Define linking.

[2+2+6+4+4+2]

- 5. a. Briefly State the characteristics of Primary device and secondary device.
 - b. Why is compiler required? Why is it important to standardize a language.
 - c. Write short notes on any two types of System software.
 - d. State the advantages and limitations of machine languages?

[5+2+3+5+5]

- 6. a. Draw the circuit diagram of 2x1 MUX using basic gates. Perform 87-25 using 2's complement arithmetic
 - b. Write down the characteristic expression of J-K Flip Flop. Show how a J-K Flip Flop converted into a T- Flip Flop.
 - c. Explain the working of Master Slave J-K Flip-Flop with a circuit diagram.

[3+4+3+4+6]

- 7. a. Design a synchronous counter using T flip flop which will count the following sequence ,
 - 1-3-5-7-1-3....Draw the appropriate circuit diagram along with excitation table.
 - b. Design a multiplier to multiply two 2 bit binary numbers using a suitable decoder.
 - c. Design a 16x1 multiplexer using only 4x1 multiplexers. Draw the appropriate circuit diagram

[(5+5)+5+5]

- 8. a. Name four registers of digital computer and explain their functions.
 - b. Explain DMA transfer in a computer system with a diagram.
 - c. Explain the operating principal of direct mapping of cache memory.

[4+(5+3)+8]

- 9. a. Compare and contrast between I/O mapped I/O and memory mapped I/O.
 - b. What is addressing mode? Explain any five addressing modes with examples.
 - c. What do you mean by bus arbitration? Explain polling and independent requesting Bus arbitration schemes briefly with proper diagram. [3+2+8+(1+3+3)]

Send the Scanned answer scripts to the following mail id: csexam.cmsa3@gmail.com