

**GURUDAS COLLEGE**  
**DEPARTMENT OF COMPUTER SCIENCE**  
**SEM – I**  
**PAPER –CMS-G-CC1-TH**

**Time: 1 hour**

**Full marks:30**

**Answer Question 1 and any four from Question 2 to 9**

- |  |             |
|--|-------------|
| 1. <b>ANSWER ANY FOUR .</b>  | 1.5 X 4 = 6 |
| a. Define data and Information.  |             |
| b. What are the full forms of ASCII and EBCDIC?  |             |
| c. What are combinational circuits?  |             |
| d. What are Minterm.   |             |
| e. Define weighted code  |             |
| f. Define Virus.   |             |
| g. Difference between Level trigger and Edge trigger.  |             |
| h. State two differences between latch and a Flip flop.  |             |
| 2. What is Gray code? Design a convertor circuit.  | 2+4         |
| 3. Prove NAND as universal gate.   | 6           |
| 4. State the main characteristic of machine language, assembly language and high level language.       | 6           |
| 5. Simplify the following Boolean function using K-Map<br>$F(A,B,C,D)= \Sigma m(1,3,4,9,10)+d(2,7,12)$ | 6           |
| 6. State and Prove De Morgan's Theorem   | 6           |
| 7. Subtract 37H from 3FH. Design Half adder using NAND gates   | 6           |
| 8. Implement 4 to 1 Mux using two 2 to 1 Muxes   | 6           |
| 9. Design a JK Flip flop   | 6           |